

Experiment 4 – Integrated System

Seyed Mohammad Amin Atyabi

810198559

Abstract – This document is Seyed Mohammad Amin Atyabi report on experiment 3 for Digital Logic Design Lab. In this experiment we are to create a frequency multiplier and exponential accelerator and a wrapper for this module.


Keyword – Frequency Multiplier, Exponential Accelerator, SOC, Wrapper, Integrated Circuit

I. INTRODUCTION


System on Chip is an integrated circuit that integrates multiple components including digital, analog, hardware and software programs all in a single chip. The main core of SoC is a processor that handles different computational tasks within the system. In addition to the processor, the system includes a memory, Input/Output ports and accelerators. Because accelerators are responsible for a single job, they can work with higher frequency than main processor. In this experiment we are about to create an exponential accelerator and a frequency multiplier to boost the frequency for our accelerator.

II. FREQUENCY MULTIPLIER

State Diagram)

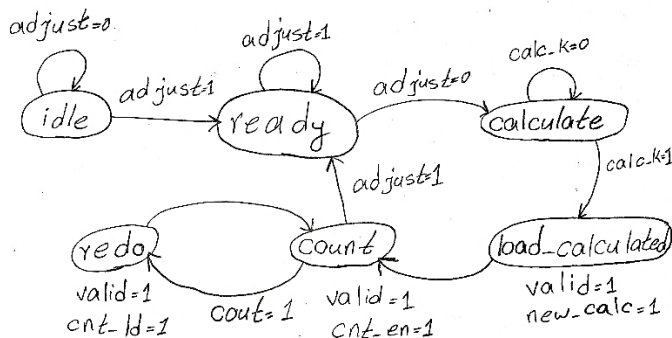


$n = 1)$

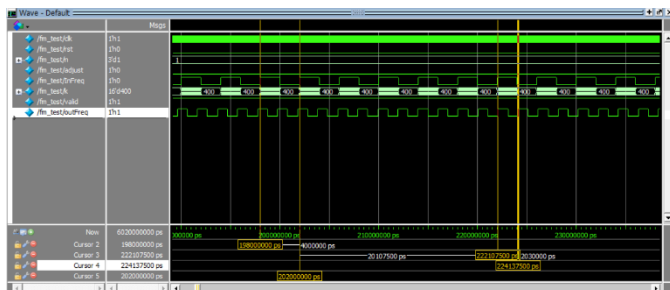


InFreq frequency = 250 KHz
outFreq frequency \approx 492 KHz

$n = 3)$

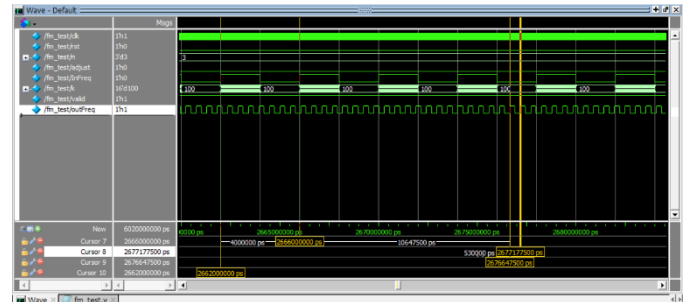

InFreq frequency = 250 KHz
outFreq frequency \approx 1.88 MHz

$n = 7)$

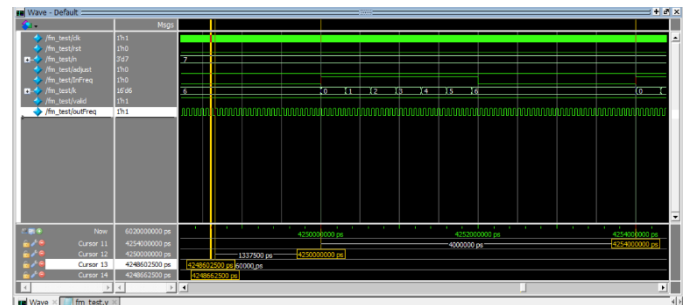


InFreq frequency = 250 KHz
outFreq frequency \approx 16.6 MHz

III. EXPONENTIAL ACCELERATOR

1. Exponential Engine

Waveform)

 

Synthesize Report)

Flow Summary	
Flow Status	Successful - Fri Jun 18 17:42:43 2021
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	exponential
Top-level Entity Name	exponential
Family	Cyclone IV E
Total logic elements	102 / 6,272 (2 %)
Total combinational functions	100 / 6,272 (2 %)
Dedicated logic registers	60 / 6,272 (< 1 %)
Total registers	60
Total pins	38 / 92 (41 %)
Total virtual pins	0
Total memory bits	0 / 276,480 (0 %)
Embedded Multiplier 9-bit elements	2 / 30 (7 %)
Total PLLs	0 / 2 (0 %)
Device	EP4CE6E22C6
Timing Models	Final

Maximum Frequency)


Slow 1200mV 85C Model Fmax Summary

	Fmax	Restricted Fmax	Clock Name	Note
1	162.95 MHz	162.95 MHz	clk	


Maximum Frequency = 162.95 MHz

2. Exponential Accelerator Wrapper


State Diagram)

 

Final Circuit)

 

Wave form)

 

Synthesize Report)

Flow Summary	
Flow Status	Successful - Sat Jun 19 12:41:30 2021
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	wrapper
Top-level Entity Name	wrapper
Family	Cyclone IV E
Total logic elements	194 / 6,272 (3 %)
Total combinational functions	186 / 6,272 (3 %)
Dedicated logic registers	118 / 6,272 (2 %)
Total registers	118
Total pins	47 / 92 (51 %)
Total virtual pins	0
Total memory bits	84 / 276,480 (< 1 %)
Embedded Multiplier 9-bit elements	2 / 30 (7 %)
Total PLLs	0 / 2 (0 %)
Device	EP4CE6E22C6
Timing Models	Final

Maximum Frequency)


Slow 1200mV 85C Model Fmax Summary

	Fmax	Restricted Fmax	Clock Name	Note
1	160.72 MHz	160.72 MHz	clk	

Maximum Frequency = 160.72 MHz

IV. FREQUENCY MULTIPLIER

Final Circuit)

 

Synthesize Summary)

Flow Summary	
Flow Status	Successful - Sat Jun 19 15:20:52 2021
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	integrated
Top-level Entity Name	integrated
Family	Cyclone IV E
Total logic elements	321 / 6,272 (5 %)
Total combinational functions	312 / 6,272 (5 %)
Dedicated logic registers	172 / 6,272 (3 %)
Total registers	172
Total pins	53 / 92 (58 %)
Total virtual pins	0
Total memory bits	84 / 276,480 (< 1 %)
Embedded Multiplier 9-bit elements	2 / 30 (7 %)
Total PLLs	0 / 2 (0 %)
Device	EP4CE6E22C6
Timing Models	Final

Wave Form)

